DESIGN CONSIDERATIONS AM TRANSMITTERS



Overview

Design Criteria

Modulation

TX Block Diagram

RF Amplifier

Harmonic Filter

Combiner

Modulator

Exciter

Power Supply

Circuit Board

Cooling

Protection



Early conceptual design starts with knowing a desired RF output power and knowing the Regulatory Requirement governing the broadcast signal such as:

- CE RED
- FCC CFR47 Part 73
- Innovation, Science and Economic Development Canada BETS5

These regulations govern items such as occupied bandwidth, spurious and harmonic emissions, Audio quality, AM noise, FM noise, Electromagnetic compatibility, safety.



Other design considerations include:

- Reliability
- Redundancy
- Dollars per watt (\$/W)
- Power density (W/in³)
- Power conversion efficiency (operating cost)
- Feature set

These considerations can quite often conflict with each other such as redundancy and \$/W.

Designers must understand and choose their guiding principals



Nautel has always considered reliability one of the leading design principal and as such has an internal engineering document guiding our acceptable component stress.

Electrical stress, at its essence comes from two parameters:

- Voltage (Joules/coulomb) stress causing dielectric breakdown and dielectric heating
- Current (Coulombs/second) stress causing excessive heating of conductors (P= i²R)



Examples of Nautel design guidelines include:

- Resistors not to dissipate more than 50% of manufactures rating
- Capacitors operating voltage to be 66% of rating
- Voltage stress in air to be 5V/mil (breakdown at sea level occurs at 75V/mil in a uniform field)
- Transistor junction temperature not to exceed 75% of max rating under normal operating conditions

These guidelines have helped establish a history of highly reliable transmitters.



Reliability and redundancy have also greatly influence Nautel designs. Going back to our roots, it was a request for improved MTBF that drove the first solid state designs as the Nav Canada needed ultra reliable transmitters in northern Canada which tube designs of the day could not meet.



We continue to build the majority of our design redundancy in mind including:

- multiple parallel amplifiers that can be hot serviced
- dual exciters
- dual low voltage power supplies
- Multiple parallel cooling fans




Nautel also uses IPC standards to guide the construction of all electronic assemblies.



Association Connecting Electronics Industries



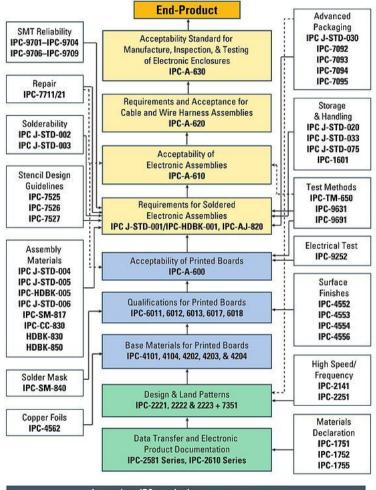
IPC STANDARDS — EVERYTHING YOU NEED FROM START TO FINISH



Learn about IPC standards at www.ipc.org/standards

DECEMBER 2014

Generic Transmitter Block Diagram

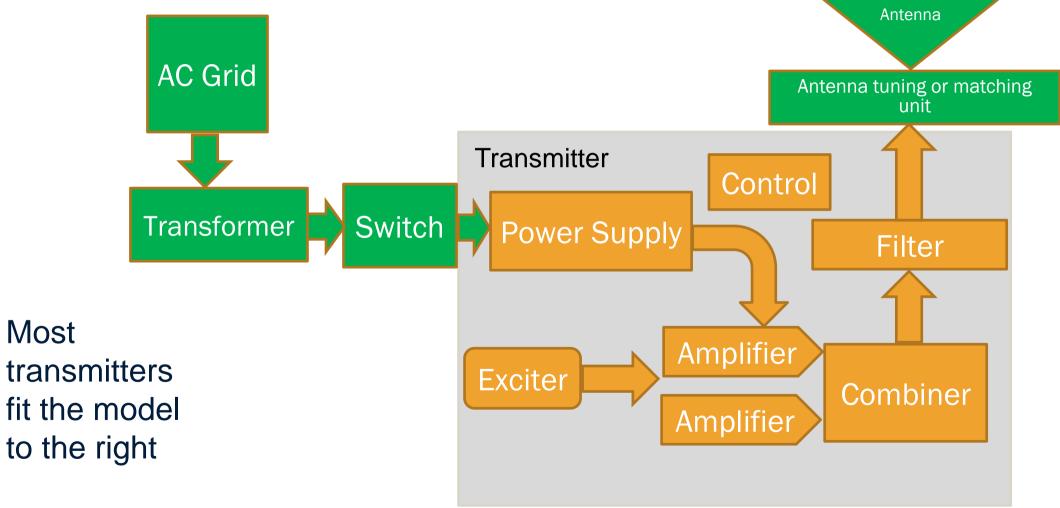



- Modulation techniques
 - Linear amplification
 - Single Pulse Duration Modulation (PDM)
 - Bi-Phase Pulse Duration Modulation (PDM)
 - Multi Phase Pulse Duration Modulation (PDM)
 - Pulse Step Modulation
 - Pulse Step Modulation with step interpolation



$$e = (1 + M \sin \omega_m t) \cdot \sin(\omega_c t)$$

Where

M is modulation index $\sin \omega_m$ t is modulating frequency $\sin(\omega_c t)$ is the carrier frequency



Consider a carrier wave (sine wave) of frequency f_c and amplitude A given by:

$$c(t) = A \cdot \sin(2\pi f_c t)$$

Let m(t) represent the modulation waveform. For this example, we shall take the modulation to be simply a sine wave of a frequency f_m , a much lower frequency (such as an audio frequency) than f_c :

$$m(t) = M \cdot \cos(2\pi f_m t + \phi)$$

where M is the amplitude of the modulation. We shall insist that M<1 so that (1+m(t)) is always positive. If M>1 then overmodulation occurs and reconstruction of message signal from the transmitted signal would lead in loss of original signal. Amplitude modulation results when the carrier c(t) is multiplied by the positive quantity (1+m(t)):

$$y(t) = [1 + m(t)] \cdot c(t)$$
$$= [1 + M \cdot \cos(2\pi f_m t + \phi)] \cdot A \cdot \sin(2\pi f_c t)$$




Using trig identities, y(t) can be shown to be the sum of three sine waves:

$$y(t) = A \sin(2\pi f_c t) + rac{1}{2} Am \left[\sin(2\pi \left[f_c + f_m
ight] t + \phi
ight) + \sin(2\pi \left[f_c - f_m
ight] t - \phi
ight)
ight].$$


Therefore, the modulated signal has three components: the carrier wave c(t) which is unchanged, and two pure sine waves (known as sidebands) with frequencies slightly above and below the carrier frequency fc.



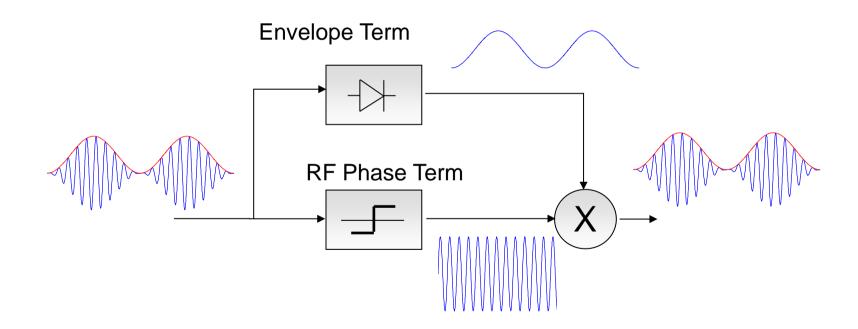Envelope Elimination and Restoration a.k.a. Kahn Technique






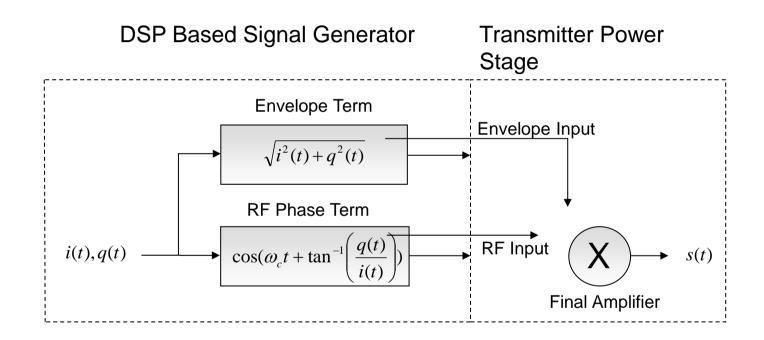




AM Transmitter Block Diagram

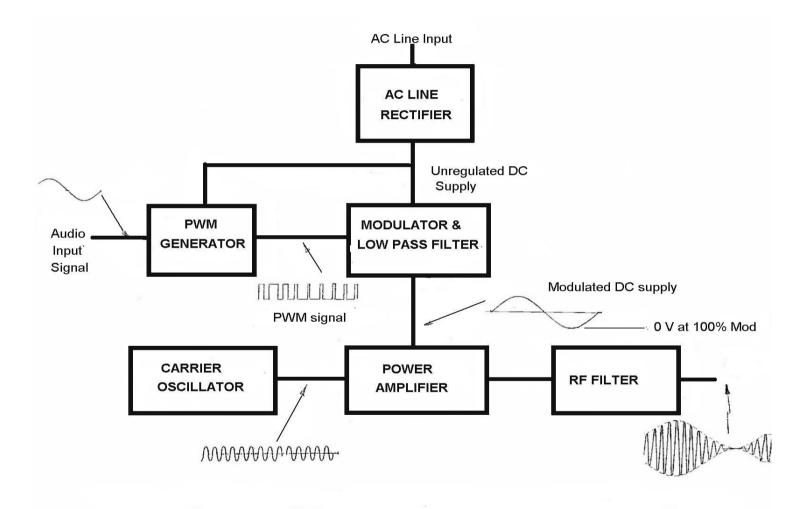



AM Transmitter Block Diagram

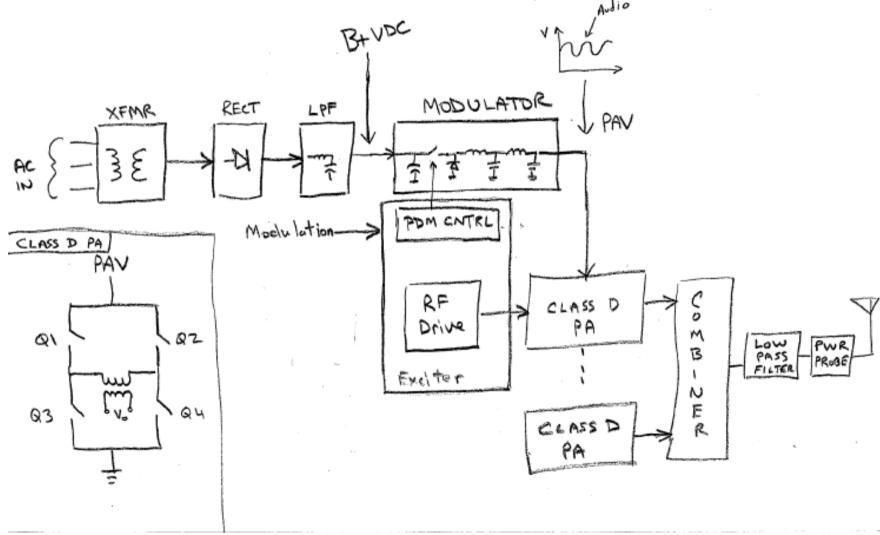



The RF amplifier design is critical to the transmitter's \$/W, W/in³, efficiency and reliability.

Usually the amplifier will be the building block of a family of models.

The power capability needs to be large enough to minimize combiner and connectors costs but small enough not to drastically affect power capability under failure. Shipping and servicing weights are also very important.



Class D amplification has been the topography of choice since the early 1980's. Class D has excellent efficiency (theoretically 100%), good \$/W and W/in³

Choosing the switching device for the full bridge is critical as well.


Drain current, input capacitance, output capacitance, dv/dt rating, thermal impedance of junction to case, case mechanics are all considered.

The amplifier is designed always to be working into an inductive load to minimize the switching loss and dv/dt.



$$f(x) = \frac{4}{\pi} \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{n} \sin\left(\frac{n\pi x}{L}\right).$$

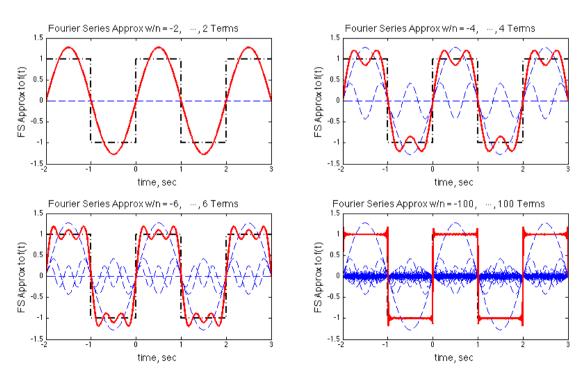Square wave produced by Class D has a fundamental and many odd harmonics






Amplifier efficiency is affected by 2 factors:

- FET on resistance (i²R_{DSon})
- Switching loss (1/2CV²F)


R_{DSon} can be minimized by choosing a high current FET

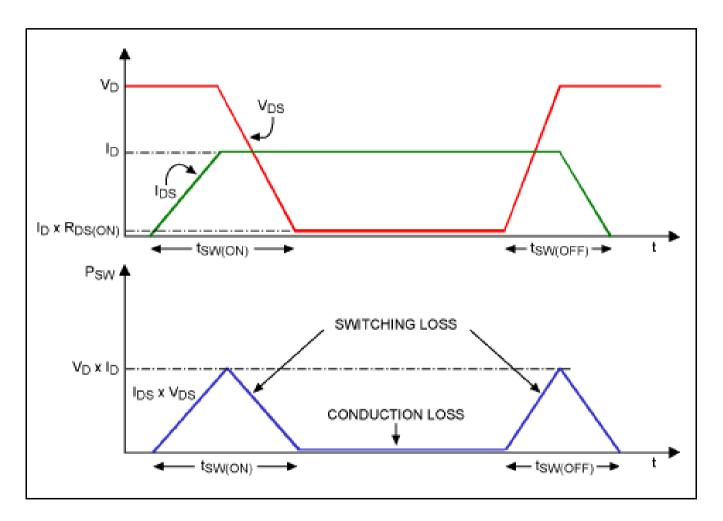Switching loss can be minimized by reducing the voltage across the FET during turn on – this is accomplished by an inductive load also known as zero voltage switching (ZVS)







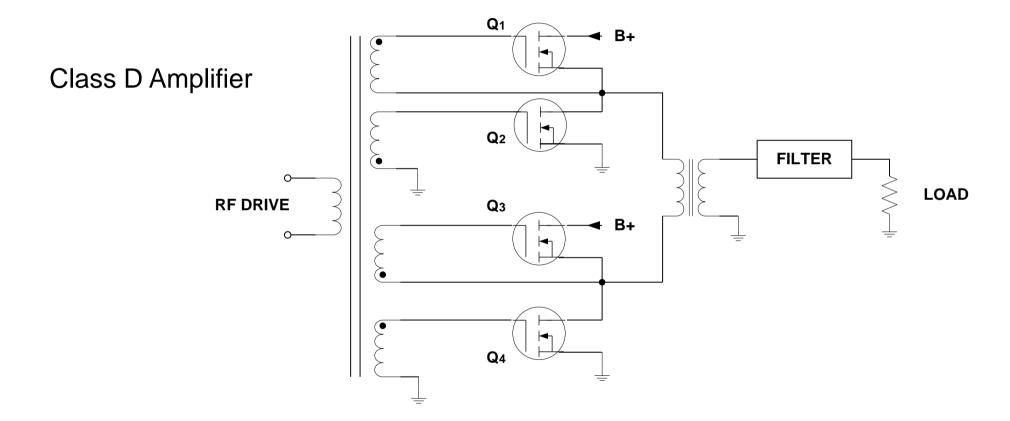



Design sequence (iterative)

- 1) FET selection determines B+ (BVdss x derating)
- 2) Modulation depth selection determines PAV {PAV=B+/(mod+1)}
- 3) TX TPO and # of RF modules determine power per module
- 4) System impedance, # of RF modules and combiner turns ratio determines filter input impedance and PA impedance
- 5) Filter input impedance determines filter component values

Power = Voltage²/resistance PA testing and analysis to ensure PA power is reliable




Typical values for NX50

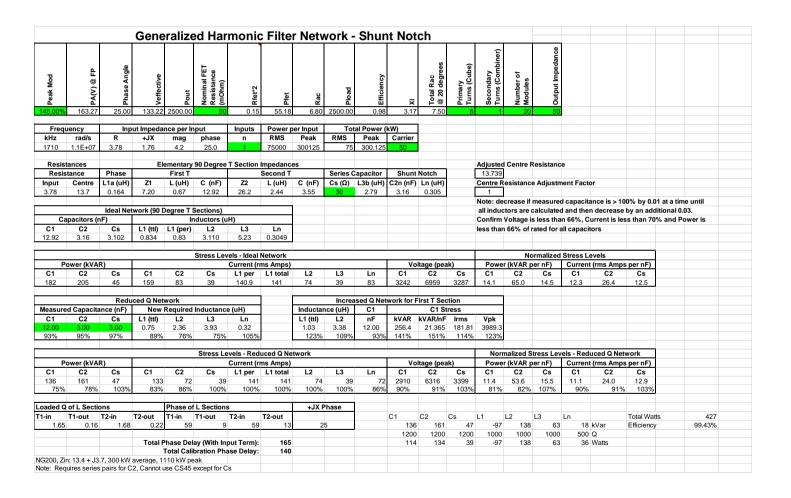- 1) B+=400VDC
- 2) PAV=163VDC
- 3) MOD Depth =145%
- 4) # of RF modules =20
- 5) Filter input Impedance = $4.17\Omega < 25^{\circ}$ or $4.60\Omega // + j9.87\Omega$
- 6) Primary Turns = 6
- 7) PA impedance= 8.28Ω //+j17.77 Ω
- 8) PA Power = $146V \ rms^2 / 8.28\Omega = 2574 \text{watts}^*$
- 9) 2574watts x 20= 50kW

^{*}don't forget square wave to sine conversion $(4/\pi)$ and peak to RMS (1/sqrt2)



Engineering has designed a spreadsheet to execute the required calculations efficiently





FET chosen for NX



APT50M50JFLL

500V 71A 0.050Ω

POWER MOS 7® FREDFET

Power MOS 7° is a new generation of low loss, high voltage, N-Channel enhancement mode power MOSFETS. Both conduction and switching losses are addressed with Power MOS 7° by significantly lowering R_{DS(ON)} and Q_g. Power MOS 7° combines lower conduction and switching losses along with exceptionally fast switching speeds inherent with APT's patented metal gate structure.

- Lower Input Capacitance
- Lower Miller Capacitance
- Lower Gate Charge, Qg
- Increased Power Dissipation
- Easier To Drive
- Popular SOT-227 Package
- FAST RECOVERY BODY DIODE







MAXIMUM RATINGS

All Ratings: T_C = 25°C unless otherwise specified.

Symbol	Parameter	APT50M50JLL	UNIT	
V _{DSS}	Drain-Source Voltage	500	Volts	
Ь	Continuous Drain Current @ T _C = 25°C	71	Amps	
I _{DM}	Pulsed Drain Current ⁽¹⁾	284		
v _{GS}	Gate-Source Voltage Continuous	±30	Volts	
V _{GSM}	Gate-Source Voltage Transient	±40		
P _D	Total Power Dissipation @ T _C = 25°C	595	Watts	
	Linear Derating Factor	4.76	W/°C	
T_{J}, T_{STG}	Operating and Storage Junction Temperature Range	-55 to 150	- °c	
TL	Lead Temperature: 0.063" from Case for 10 Sec.	300		
I _{AR}	Avalanche Current (Repetitive and Non-Repetitive)	71	Amps	
E _{AR}	Repetitive Avalanche Energy ①	50	mJ	
E _{AS}	Single Pulse Avalanche Energy (3)	3200		



STATIC ELECTRICAL CHARACTERISTICS

Symbol	Characteristic / Test Conditions	MIN	TYP	MAX	UNIT
BV _{DSS}	Drain-Source Breakdown Voltage $(V_{GS} = 0V, I_D = 250\mu\text{A})$	500			Volts
R _{DS(on)}	Drain-Source On-State Resistance ② (V _{GS} = 10V, 35.5A)			0.050	Ohms
I _{DSS}	Zero Gate Voltage Drain Current (V _{DS} = 500V, V _{GS} = 0V)			100	μА
	Zero Gate Voltage Drain Current (V _{DS} = 400V, V _{GS} = 0V, T _C = 125°C)			500	
I _{GSS}	Gate-Source Leakage Current (V _{GS} = ±30V, V _{DS} = 0V)			±100	nA
V _{GS(th)}	Gate Threshold Voltage (V _{DS} = V _{GS} , I _D = 5mA)	3		5	Volts

CAUTION: These Devices are Sensitive to Electrostatic Discharge. Proper Handling Procedures Should Be Followed.

APT Website - http://www.advancedpower.com




Harmonic filter needs to impedance match the antenna to the amplifier to achieve designed power. $(4.17\Omega < 25^{\circ})$ to 50Ω

The harmonic filter needs to attenuate harmonics produced in the amplifiers.

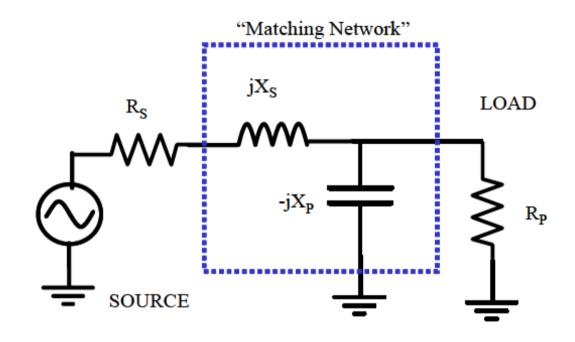The harmonic filter needs to provide isolation from external energy which could damage the amplifiers.






$$X_S = Q R_S$$


$$X_p = R_p / Q$$


We can know Q because:
$$Q^2 + 1 = \frac{R_P}{R_S}$$
 or $Q = \sqrt{\frac{R_P}{R_S}} - 1$




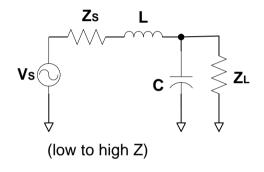L Networks are used to step up or step down impedance



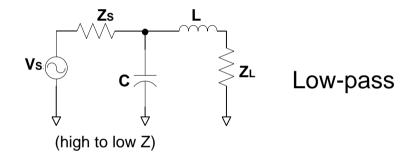


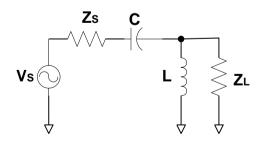

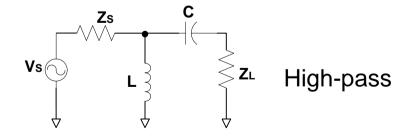




T networks are back to back L networks

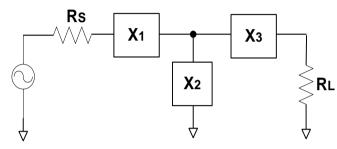

Three-element T Network

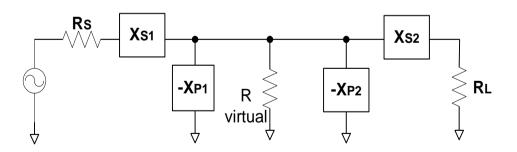



Harmonic filter uses a double Tee with 3rd notch design to reduce harmonics and impedance match the RF amp to the antenna. Double Tee has the advantage of :

- keeping impedance matched as shunt C drifts with temperature
- Wide bandwidth
- Good attenuation

A series capacitor and shunt coil provide static and low freq transient protection as well as transient suppressor device.



Combiner

The combiner needs to efficiently add the RF modules powers while providing isolation between inputs.

Combiners can be categorized as those with balancing resistors and those without.

Number of inputs needs to be greater than 4 for combiners without balancing resistors in ordered for reasonable isolation under failure.



Combiner

AM, for several generations, has used combiners without balancing resistors.

AM Combiners have been both parallel (60°) and series.


Ampfet, NX = series

ND, XL, XR, NA= parallel

Series combining is broadband, less expensive, and uses a smaller footprint




Combiner/Harmonic Filter

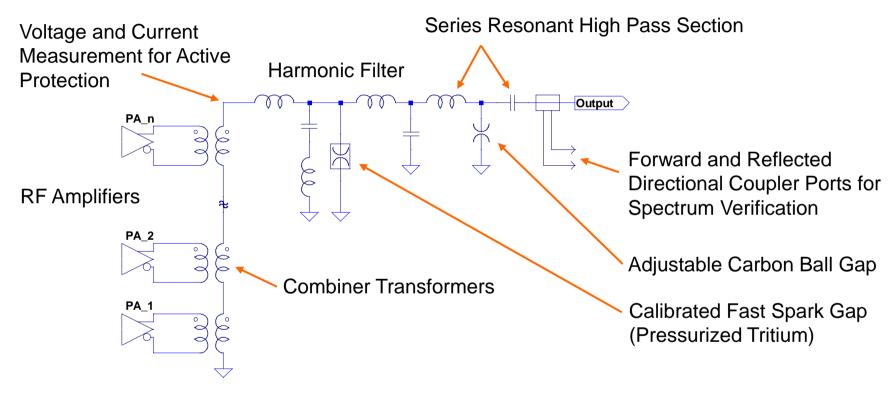

Frequency Agile: Harmonic Filter Re-Tune in a Few Hours




Pulse Width Modulator

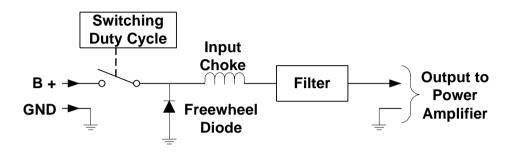

- This circuit illustrates the simple switched modulator principle. It applies a fixed DC supply voltage B+ through a series switch to a low pass filter.
- The switch is opened and closed at a fixed frequency of approximately 70kHz producing a square wave with a peak value of B+ at the filter input.
- The filter rejects the 70kHz signal and produces a dc voltage at its output equal to the average value of the square wave
 - Example: one half of B+ for a 50/50 duty cycle.
- If the duty cycle is slowly varied, the DC output voltage may be adjusted from 0 to B+.




Origins of PWM Generator

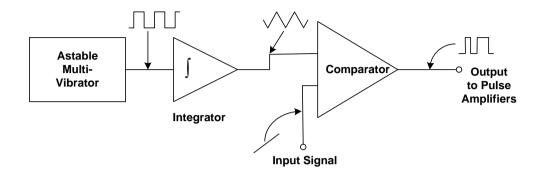

- 70kHz multi-vibrator can be passed to an integrator to produce the required saw-tooth waveform.
- If an audio modulating signal is superimposed on the control voltage, then the width of the pulses in the PWM control signal will vary accordingly.
- Waveforms depicting this process are shown on the next slide.
- It is important to understand that both the RF output level and the modulation information is digitally encoded into the PWM control signal's pulse width while its repetition frequency and amplitude remain constant.




PWM Generator Waveforms

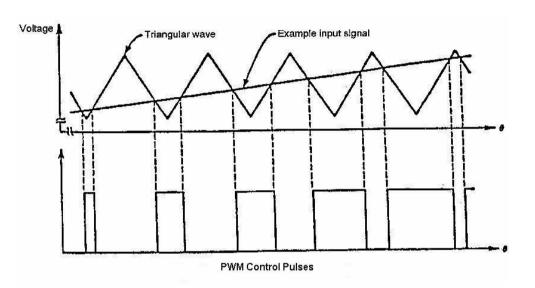

- These waveforms illustrate how the width of the PWM pulses increase in response to a rising control waveform input.
- Note the constant amplitude and repetition frequency of the PWM signal.
- The saw-tooth must have a very stable DC reference level and a very linear slope to ensure high fidelity of the transmitter's modulated output signal.



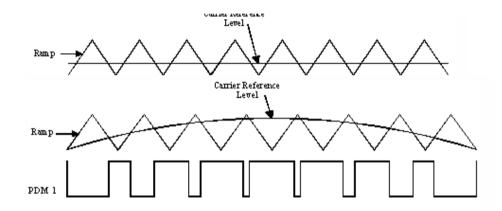
- PWM signals generated for Carrier only – no audio applied
- PDM signals generated for carrier with audio applied





 PWM signals generated for Carrier only – no audio applied

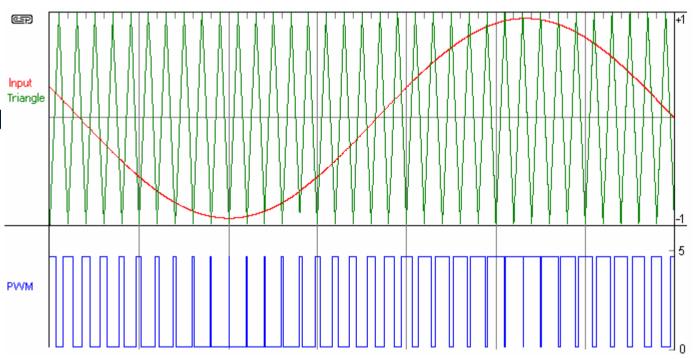 PDM signals generated for carrier with audio applied





Digital Modulation Technology

Separate power processing stages for Envelope Modulation and RF Amplification are Employed. This approach enjoys the following benefits:

- •Optimal RF Transistor switching is maintained at all modulation levels. This cannot be achieved when the RF transistors must both convert DC to RF and vary the RF envelope.
- •Digitally controlled RF Transistor switching has nearly eliminated switching loss across the AM band
- •Allows for very high current capability transistors to reduce conduction loss
- •Results in ultra high efficiency RF amplifier (up to 98% at 1710 kHz)
- •RF Amplifier DC Supply can be shut down during transient events/VSWR to further improve robustness
- •All amplifiers see the same load at all power and modulation levels



The 9 Modulation phases are separately synthesized digitally at 317 MSPS in the exciter FPGA. This results in very low quantization noise.


Each Modulator phase samples the desired envelope at a rate of over 300 kHz.

The 9 Phase process samples the envelope at over 2.7 million samples per second. This rate does not change with frequency.

Distortion due to the modulation process is essentially eliminated.


Reduced switching harmonic content allows for a very low Q modulation filter.

9 Phase Digital Modulation

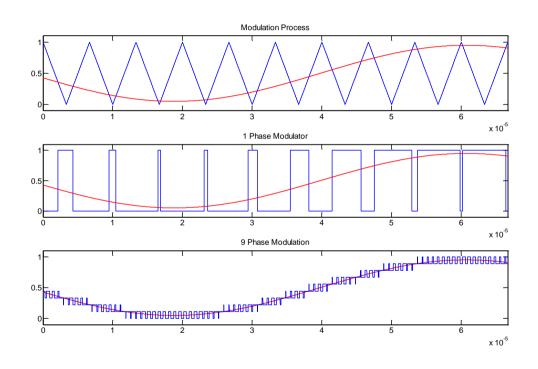



Amplifier Design

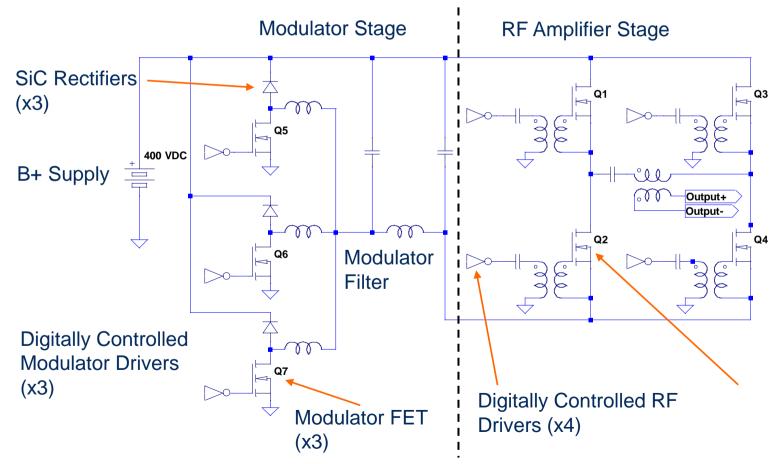



Optional Title or **Your** Logo

Making Digital Broadcasting Work.

- Exciter design has advanced greatly from early TTL and discretes to a powerful DSP and FPGA.
- The 2 signals being generated have not changed: RF drive (carrier freq) and Mod Drive (PDM)
- With the DSP, the exciter can now compensate for many of the distortions in the amplifiers and modulators.
- Modulator pinch-off, modulator filter roll-off and RF amplifier incidental phase modulation are all corrected.



"The NX Series of AM transmitters are the first high power AM transmitters to be provided with Dynamic Pre-correction"

- Corrects primary forms of distortion
- Applies to analog + digital broadcasting
- More Linear Clean Spectrum
- Adaptive envelope equalization
- Adaptive AM-AM correction
- Adaptive AM-PM correction

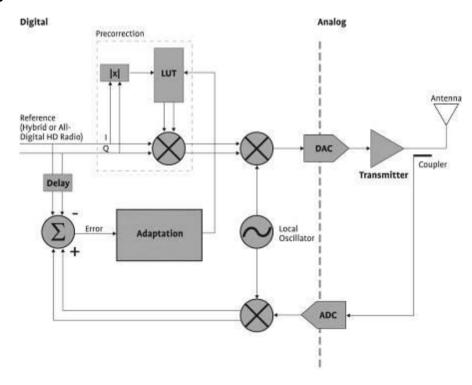
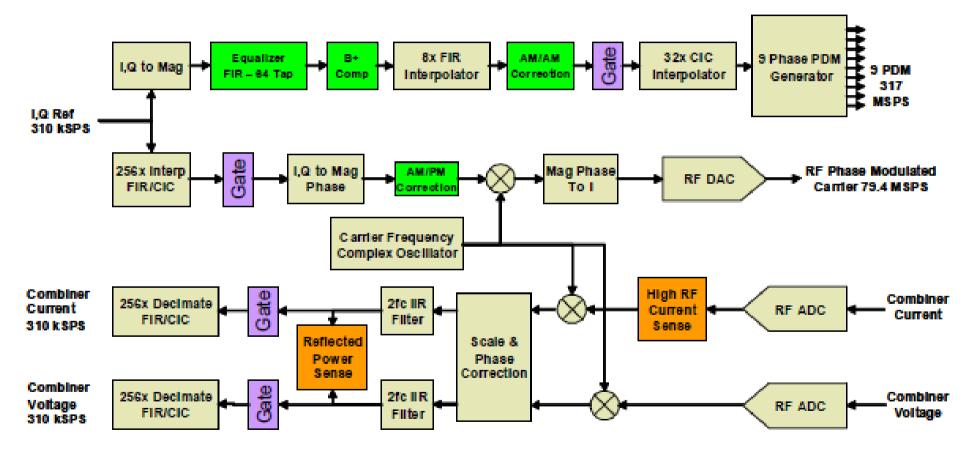


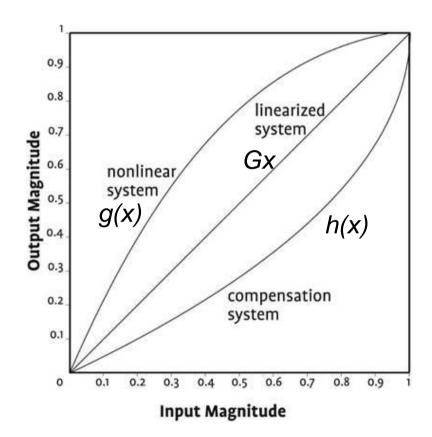


Figure 2.2: Block Diagram - FPGA






Pre-Correction Principle



An amplifier characteristic g(x) may be corrected for with a complementary characteristic h(x) such that g(h(x)) = Gx

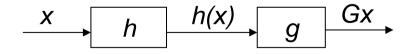For this to be true, $G h(x) = g^{-1}(x)$






The FPGA has three correction sections in the forward path:

- Envelope equalization: Corrects for filtering effects in the modulator (envelope magnitude and phase response versus frequency)
- AM/AM Correction: Corrects for amplitude error in the modulator due to capacitive effects in the modulator FET. (Essentially AM distortion)
- AM/PM Correction: Corrects for phase error in the RF amplifier due to capacitive effects in the RF FET. (IQM or IPM effects)

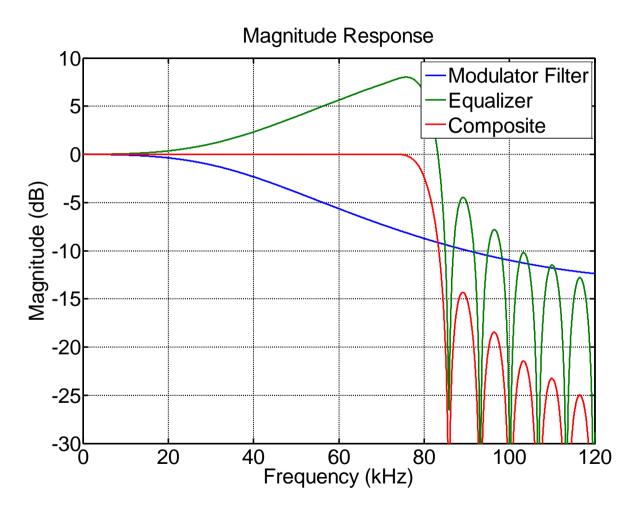
Additionally it will be possible to correct for linear effects in the AM antenna system using a filter in the DSP








AUI Screen EQ Frequency Response

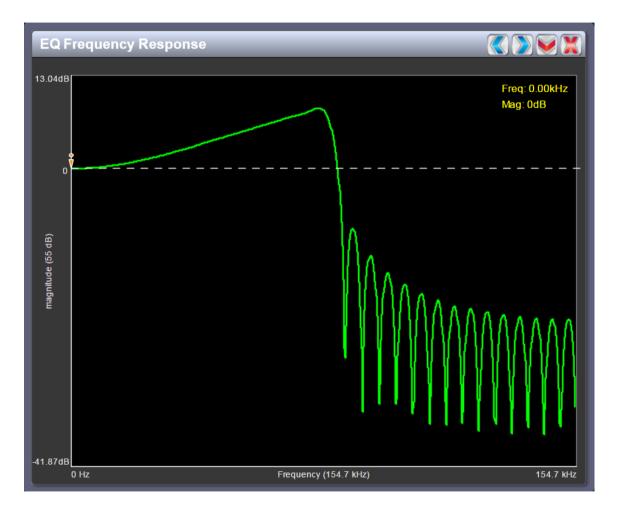



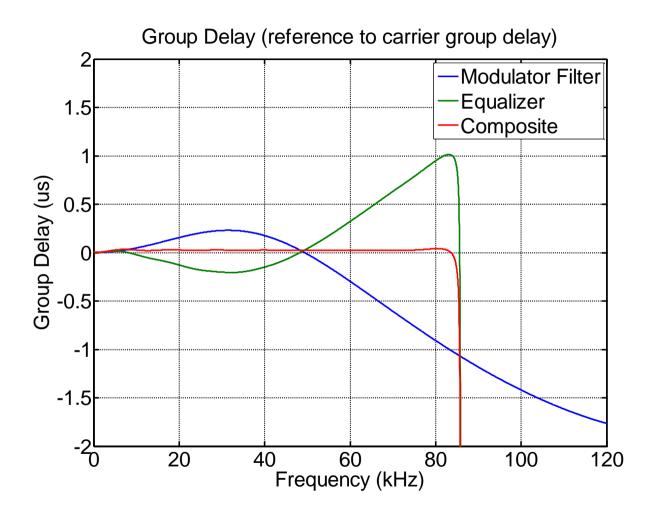




AUI Screen EQ Filter Delay






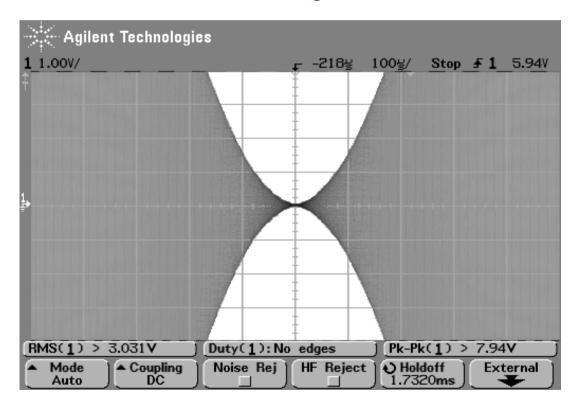No visible distortion in the trough with AM to AM correction




AUI Screen AM-AM Correction

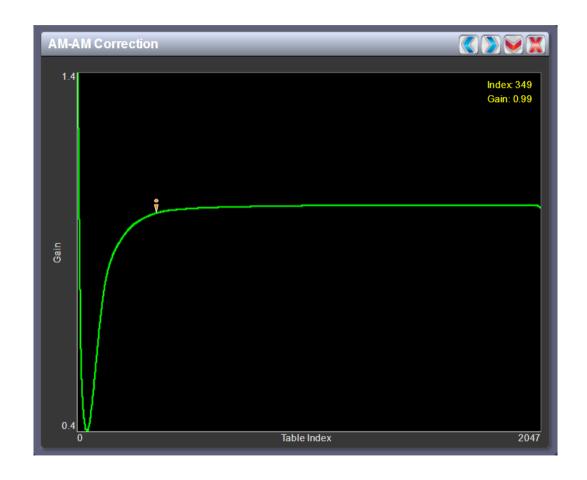




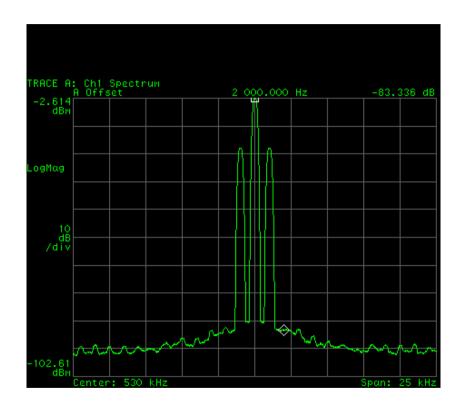
Nearly total elimination of distortion at 25% modulation (Distortion approx. 0.05%)





AUI Screen PM-AM Correction

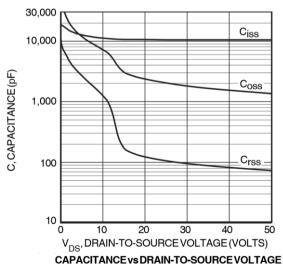

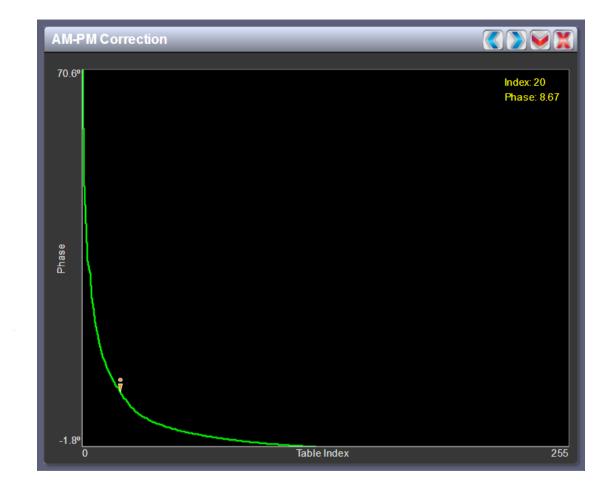



Optional Little or **Your** Logo

The AC power from the grid must be rectified so that it can be switched at the desired carrier frequency. AC/DC power conversions has two design possibilities:

- 50/60Hz rectification 'big iron'
- Switching power supplies

In a nutshell the 'big iron' is very reliable and has excellent \$/W at high power (>10kW)

Switching power supplies offer higher power density (W/in³), lower weight and higher redundancy



Regulations regarding the AM noise on the output RF signal would force the low pass filter following the rectifiers to be excessive.

Nautel patented a 'lines volt compensation' technique early on in its solid state designs that is continued to be used today.



Power supply design greatly affects the performance of the transmitter within the user's environment.


Big iron power supplies typically use SCR's for soft start and regulation but have power factor levels at approx. 0.93.



When running from generator, the transmitter's regulation circuits can make the load appear as a negative resistance causing instability in the generator's operation.

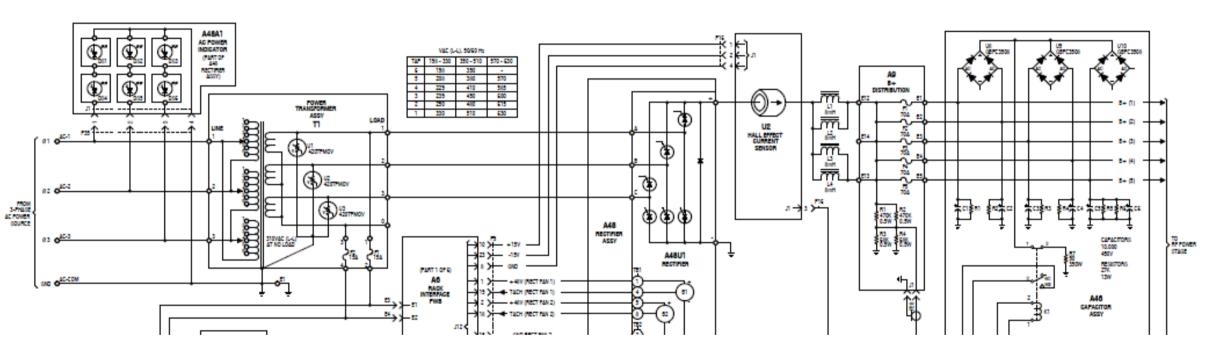Also high power rectifiers can cause 'line notching' which drastically reduces the available power from the generator.







Circuit Board Design

Circuit board creation represents a significant portion of the total transmitter design effort.

Circuit boards typically use copper cladded epoxy resin (FR-4) but sometimes employ high quality materials (ie. Teflon) depending on the application.

FR-4 can operate at approx. 90C before discolouration and delamination.

The copper cladding is quantified in 'ounces' with each ounce resulting in 0.0014" thk of copper cladding.



Circuit Board Design

Nautel has strict guidelines for the current that a PWB conductor may carry versus the ounces of copper.

In high voltage applications, there are rules on creepage and clearance distances that must be followed for maximum reliability.

Nautel has an internal 100 point checklist that every PWB must pass before being manufactured.



Cooling

Transmitters employs multiple parallel DC cooling fans which provide:

- redundancy
- high efficiency
- not sync'd to AC line frequency



Protection

Transmitter's control function provides protection such as:

- SWR protection techniques (cutback, foldback, shutback)
- Thermal protection fan tach, heatsink monitor
- Over current protection
- Over modulation protection



Thank You





